

PC measurement electronics

# **Spider8**

## **Spider8-30 and**

## **Spider8-01**

B0405-7.0 en



# Contents

|   |            |
|---|------------|
| Safety instructions .....   | 4          |
| <b>A Introduction .....</b>   | <b>A-1</b> |
| 1 Points to note about the Spider8 documentation .....                  | A-3        |
| 2 List of components supplied .....                                     | A-4        |
| 3 What is Spider8 .....   | A-5        |
| 3.1 Survey of the Spider8 family - module types .....                   | A-9        |
| <b>B Structure of the PC measurement electronics with Spider8 .....</b> | <b>B-1</b> |
| 1 Connection facilities .....   | B-3        |
| 1.1 Power supply/power pack .....                                       | B-4        |
| 1.2 Modules (carrier-frequency/DC) .....                                | B-5        |
| 2 Interfaces .....  | B-6        |
| 2.1 PC/Master .....   | B-7        |
| 2.2 Printer/Slave .....   | B-8        |
| 2.3 RS-232-C .....  | B-9        |
| 3 I / O socket .....  | B-11       |
| 4 Front panel .....   | B-15       |
| <b>C Commissioning .....</b>  | <b>C-1</b> |
| 1 Commissioning .....   | C-3        |
| 1.1 Installing modules .....  | C-4        |
| 1.2 Switching on Spider8 .....  | C-6        |
| 1.3 Installing software .....   | C-7        |

*For the sake of the environment, we print on chlorine-free paper.  
The binder and slip-case are finished in chlorine-free polypropylene film.*

|          |  |            |
|----------|--|------------|
| <b>D</b> | <b>Connecting</b>  | <b>D-1</b> |
| 1        | Shielding design   | D-3        |
| 2        | Connecting a power pack  | D-4        |
| 3        | Connecting transducers   | D-5        |
| 3.1      | S/G transducers  | D-11       |
| 3.1.1    | S/G full bridge  | D-11       |
| 3.1.2    | S/G half bridge  | D-12       |
| 3.1.3    | Single S/G using three-wire connection   | D-13       |
| 3.1.4    | Single S/G using three-wire connection   | D-14       |
| 3.1.5    | Special S/G using three-wire connection<br>(Increasing the internal compensating resistance) | D-15       |
| 3.1.6    | Special S/G using three-wire connection<br>(External compensating and shunt resistor)        | D-16       |
| 3.2      | Inductive transducers  | D-17       |
| 3.2.1    | Inductive full bridge  | D-17       |
| 3.2.2    | Inductive half bridge  | D-18       |
| 3.3      | DC voltage sources   | D-19       |
| 3.4      | DC power sources   | D-21       |
| 3.5      | Resistors  | D-22       |
| 3.6      | Potentiometer  | D-23       |
| 3.7      | Thermocouples  | D-24       |
| 3.8      | Frequency measurement / pulse counters   | D-26       |
| 4        | Connecting a PC  | D-27       |
| 4.1      | PC requirements  | D-27       |
| 4.2      | Connecting several Spider8 devices   | D-29       |
| 4.2.1    | Mixed operation for device types Spider8 and Spider8-30                                      | D-30       |
| 5        | Connecting a printer   | D-31       |

---

---

|          |   |            |
|----------|---|------------|
| <b>E</b> | <b>Configuring the Spider8 with the setup program</b> | <b>E-1</b> |
| 1        | Setup program   | E-3        |
| 1.1      | The first display                                     | E-5        |
| 1.2      | Description of the setup dialogue                     | E-11       |
| 1.3      | Mark channels   | E-20       |
| 2        | Channel-specific menus                                | E-22       |
| 3        | Device-specific menus                                 | E-30       |
| <b>F</b> | <b>Specifications</b>                                 | <b>F-1</b> |
| <b>G</b> | <b>Keyword index</b>                                  | <b>G-1</b> |
| <b>H</b> | <b>Declaration of conformity</b>                      | <b>H-1</b> |

This is a “Table of Contents preview” for quality assurance

The full manual can be found at <http://the-checkout-tech.com/estore/catalog/>

We also offer free downloads, a free keyboard layout designer, cable diagrams, free help and support.

<http://the-checkout-tech.com> : *the biggest supplier of cash register and scale manuals on the net*